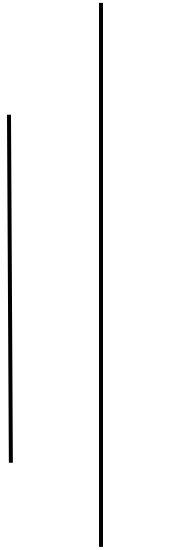




SHAHD SMARAK COLLEGE

Kirtipur, Kathmandu



Assignment no: - 5 of Digital logics

Submitted by :-

1st semester

Amir Maharjan

Submitted to :-

Himal Raj Gental

Assignment - 5

construction of ROM

- x) Design a combinational circuit using a ROM.
The circuit accepts a 3-bit number & generates an output binary number equal to the square of the input number.

X	Y	Z	F ₁	F ₂	F ₃	F ₄	F ₅	F ₆
0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	1
0	1	0	0	0	0	1	0	0
0	1	1	0	0	1	0	0	1
1	0	0	0	1	0	0	0	0
1	0	1	0	1	1	0	0	1
1	1	0	1	0	0	1	0	0
1	1	1	1	0	0	0	0	1

↳ Here, in the above truth table the combinational circuit has 3 inputs & 6 outputs.
So, the boolean function is:-

$$\text{no of inputs } (n) = 3$$

$$\text{no of outputs } (m) = 6$$

we know, that decoder is 2^n

$$\text{So, } 2^n = 2^3 = 8$$

∴ 8 to 8 decoder.

Boolean Function

$$F_1 = \Sigma(6, 7)$$

$$F_2 = \Sigma(4, 5, 6)$$

$$F_3 = \Sigma(3, 5)$$

$$F_4 = \Sigma(2, 6)$$

Now, we construct a 8×6 ROM with the help of 8 to 8 decoder.

