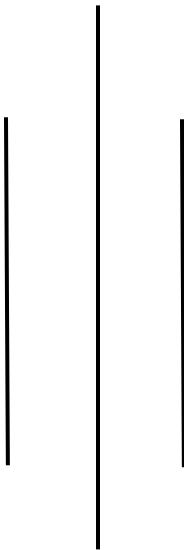




SHAID SMARAK COLLEGE

Kirtipur, Kathmandu



Assignment No. 5 of Digital logic

Submitted by :-

1st semester

Amir Maharjan

Submitted to :-

Himal Raj Gental

LAB 1 : BEING FAMILIAR WITH BASIC LOGIC GATES

Objective:

- To be familiar with basic logic gates i.e. AND, OR , NOT, XOR, NAND and NOR.
- To see how these gates are fabricated in Integrated Chips.

Equipment Needed:

- a) Breadboard
- b) 9V Battery
- c) LED Bulbs
- d) 5v Registers
- e) Jumper Wires
- f) Toggle Switches
- g) IC Names for corresponding gates

Discussion:

a) AND Gate

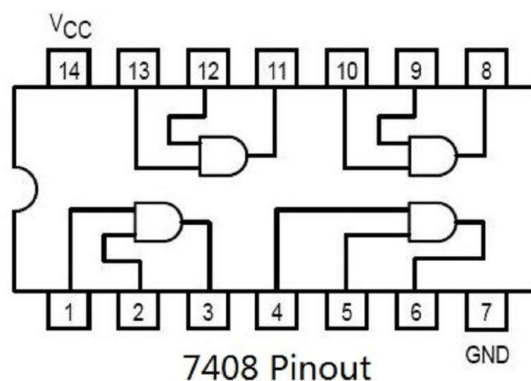


Fig: IC7408 (AND gate)

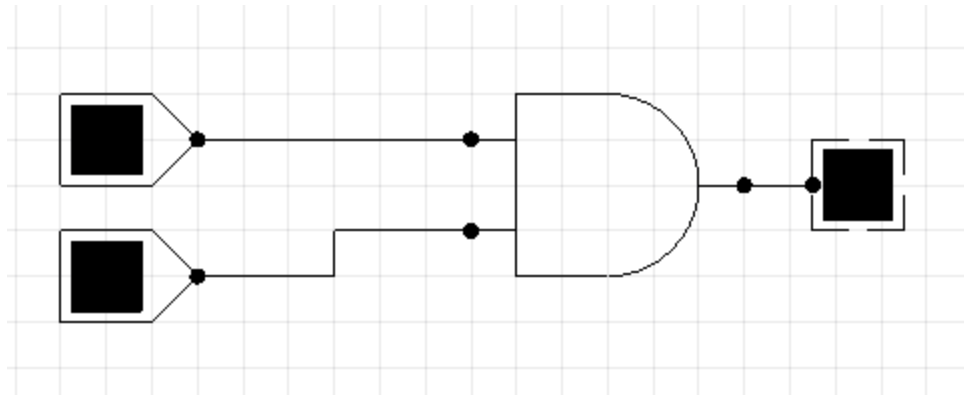


Fig: Circuit Diagram for AND gate

A	B	A.B
0	0	0
0	1	0
1	0	0
1	1	1

Fig: Observed result of AND gate

b) OR Gate

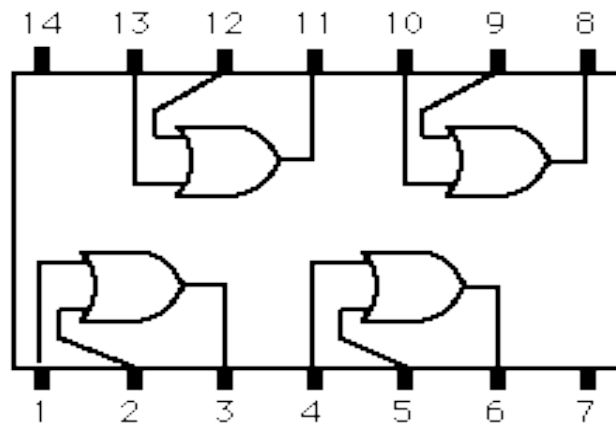


Fig: IC7432 (OR Gate)

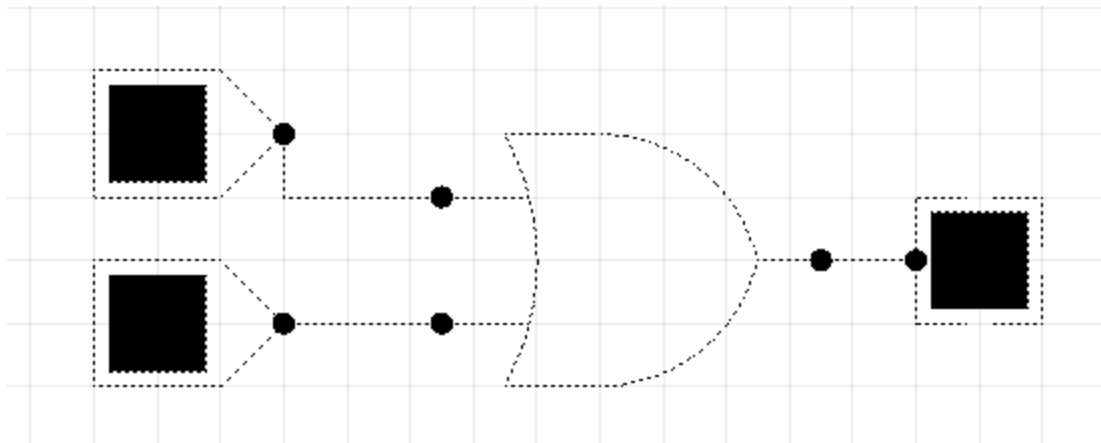


Fig: Circuit Diagram of OR Gate

A	B	X (A+B)
0	0	0
0	1	1
1	0	1
1	1	1

Truth table of OR Gate

c) NOT Gate

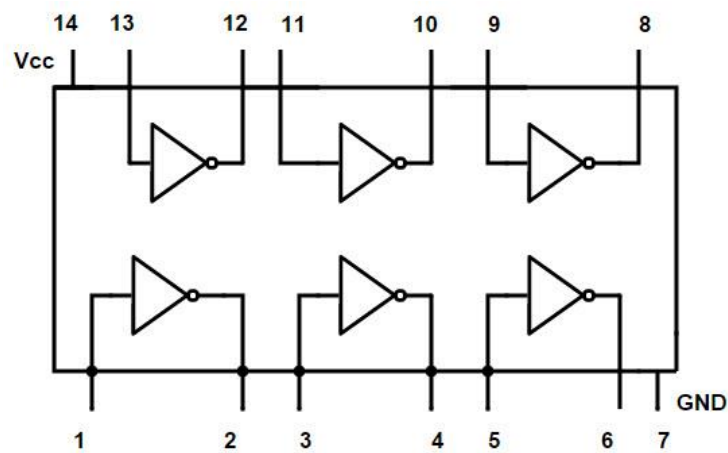


Fig: IC7404 (NOT Gate)

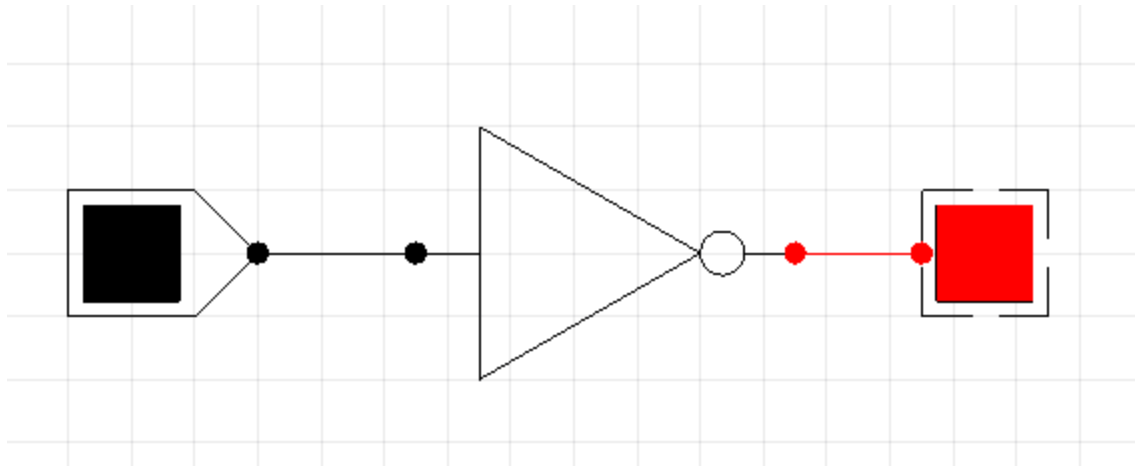


Fig: Circuit Diagram of NOT Gate

A	X
0	1
1	0

Fig: Truth Table of NOT Gate

D) NAND Gate

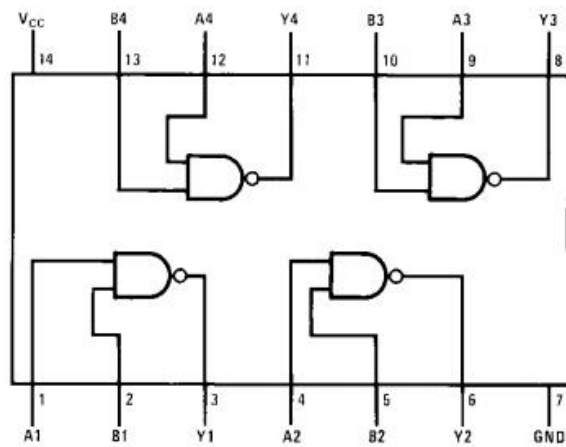


Fig: IC7400 (NAND Gate)

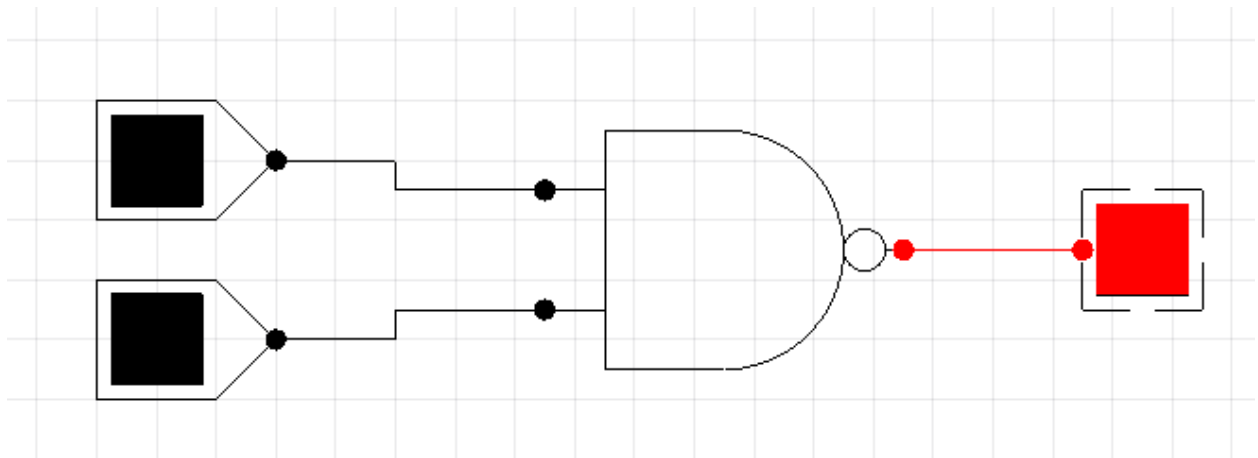


Fig: Circuit Diagram for NAND Gate

A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

Fig: Truth Table of NAND Gate

e) NOR Gate

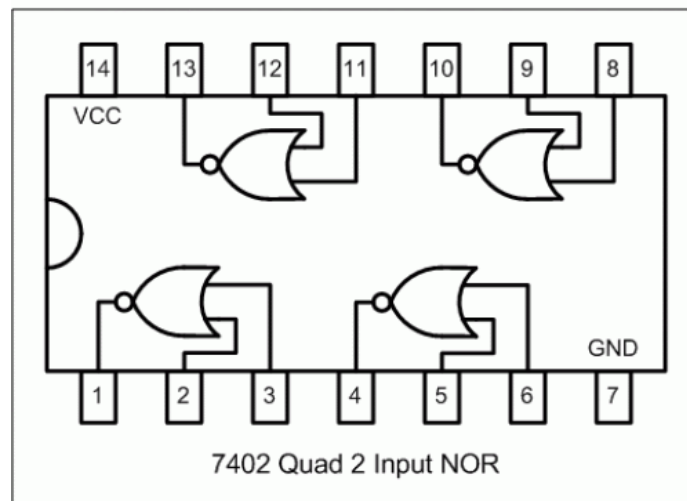


Fig: IC7402 (NOR Gate)

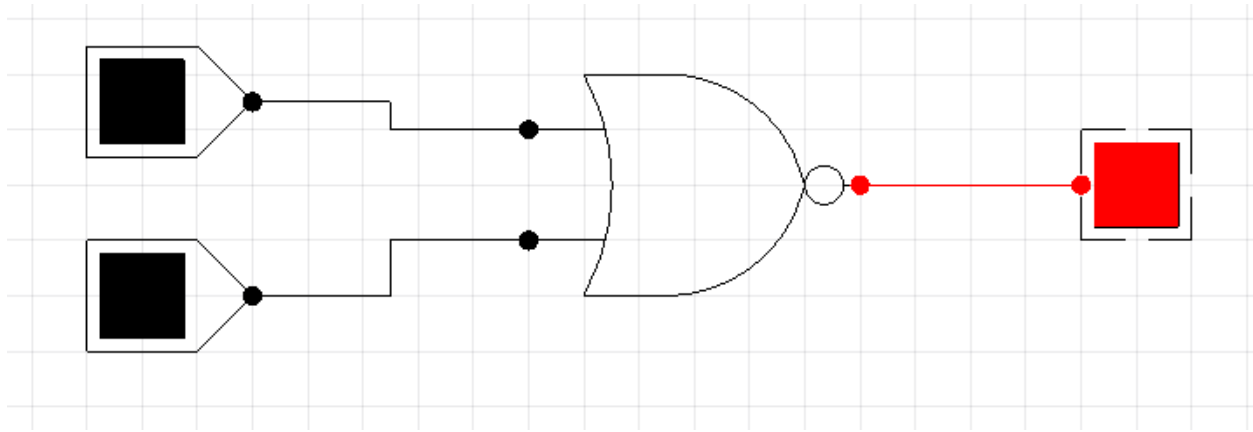


Fig: Circuit Diagram of NOR Gate

A	B	X
0	0	1
0	1	0
1	0	0
1	1	0

Fig: Truth table of NOR gate

F) XOR Gate

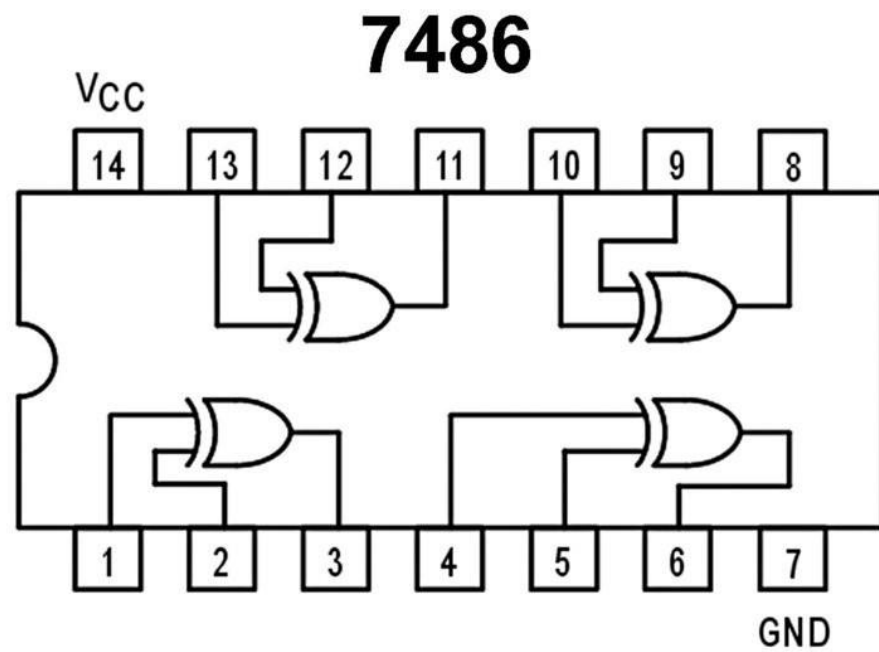


Fig: IC7486 (XOR gate)

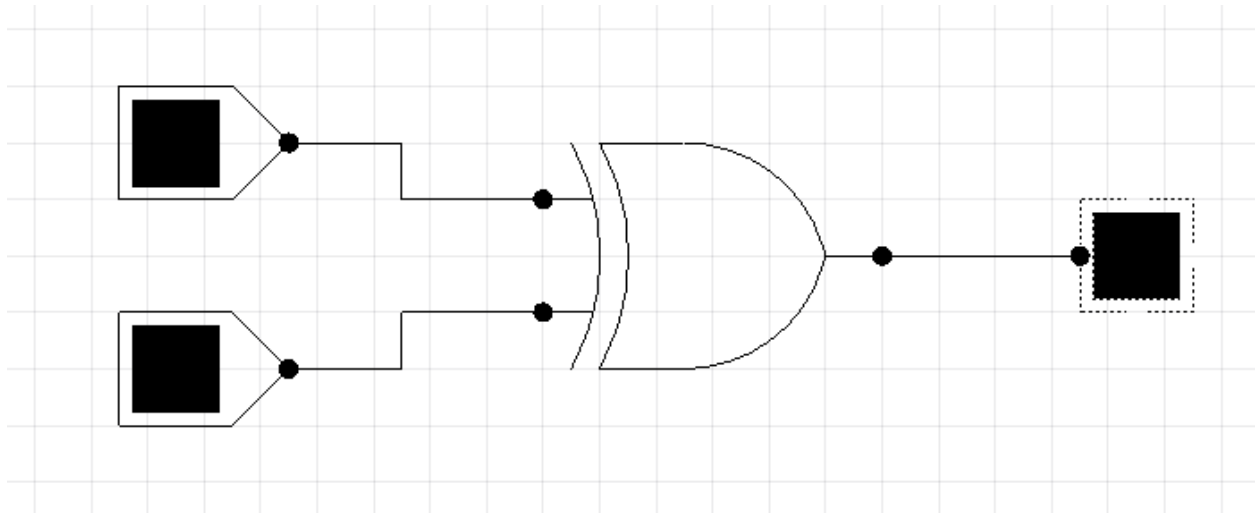


Fig: Circuit Diagram of XOR gate

A	B	X
0	0	0
0	1	1
1	0	1
1	1	0

Fig: Truth Table of XOR gate