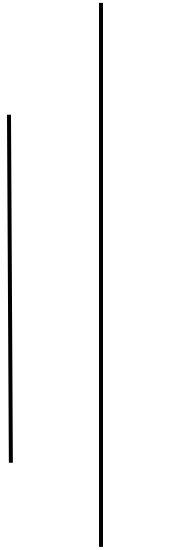




SHAHD SMARAK COLLEGE

Kirtipur, Kathmandu



Lab no: 3 of Digital logics

Submitted by :-

1st semester

Amir Maharjan

Submitted to :-

Himal Raj Gental

LAB 3: HALF-ADDER AND FULL-ADDER

Objective:

- To learn about half adders and full adders.
- To implement the half adders and full adders.

Discussion:

Digital computers perform a variety of information processing tasks. Among the basic functions encountered are the various arithmetic operations. The most basic arithmetic operation, no doubt, is the addition of two binary digits.

• Half-adders

A half adder is a type of adder, an electronic circuit that performs the addition of number. The half adder is able to add two single binary digits and provide the output plus a carry value. It has two inputs, called A and B, and two outputs S (Sum) and C (Carry).

The Truth table formulation of half-adders given below:

A	B	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Truth Table of Half adder


The simplified Boolean function for the two outputs can be obtained directly from the truth table. The simplified Sum of Products (SOP) expression are: -

$$S = X'Y + XY'$$

$$C = XY$$


After obtaining the simplified Sum of Products (SOP) expression all we have to do is implement the simplified expression.

- **Implementation**

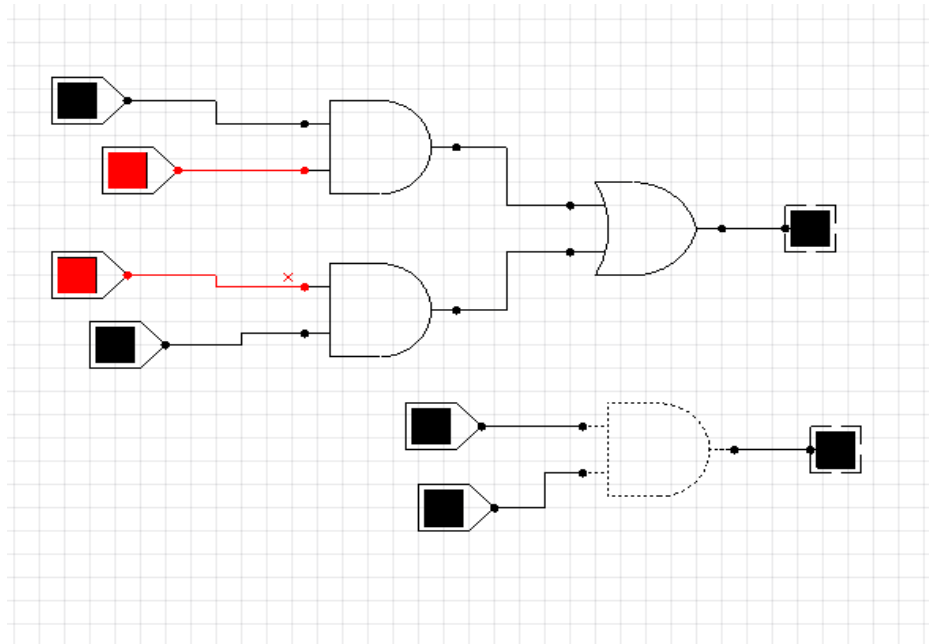


Circuit diagram of $S = X'Y + XY$, $C = XY$

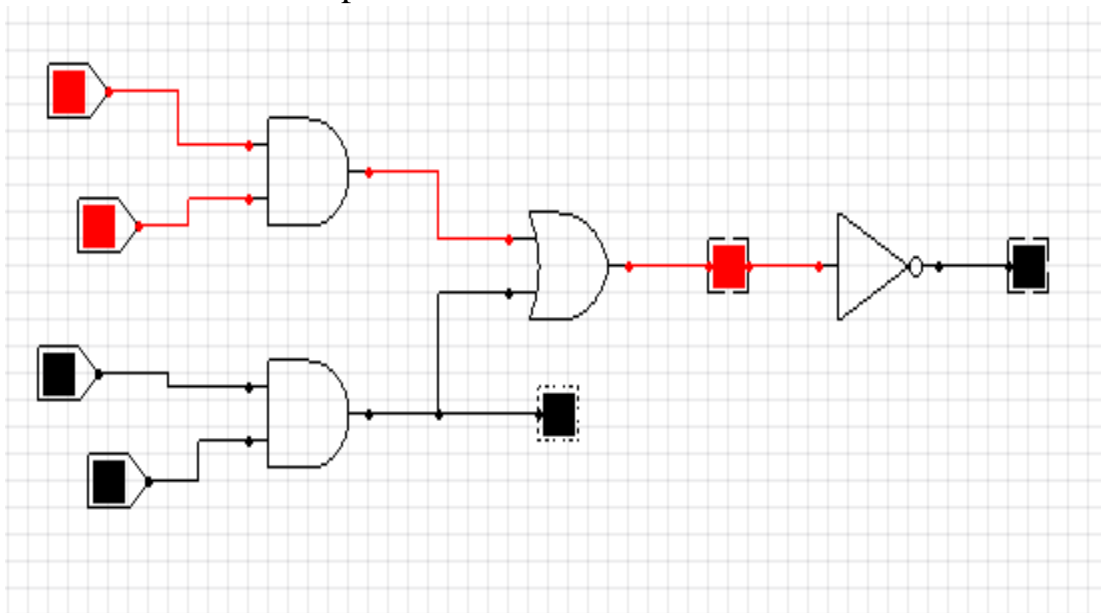Other realizations and implementation of half-adders are: -



 Circuit diagram of $S = (C + X'Y')$, $C = XY$



Circuit diagram of $S = \text{XOR gate}$, $C = XY$

- **Full adders**

Full adder is the adder which adds three inputs and produces two outputs. A full adder logic is designed in such a manner that can take eight inputs together to create a byte-wide adder and cascade the carry bit from one adder to another.

The three inputs are A, B and Z, and the two outputs are as in the half adder S (sum) and C (carry).

The truth table formulation of the full adder is given below: -

A	B	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Truth table of Full adder

The input-output logical relationship of the full adder circuit may be expressed in two Boolean functions, each one output variable. Each output Boolean function requires a unique map for its simplification.


A	BZ	00	01	11	10
0			1		1
1		1		1	

$$S = X'Y'Z + X'YZ' + XY'Z' + XYZ$$


A	BZ	00	01	11	10
0				1	
1			1	1	1

$$C = XY + XZ + YZ$$

- **Implementation**

 


$$C = XY + XZ + YZ$$

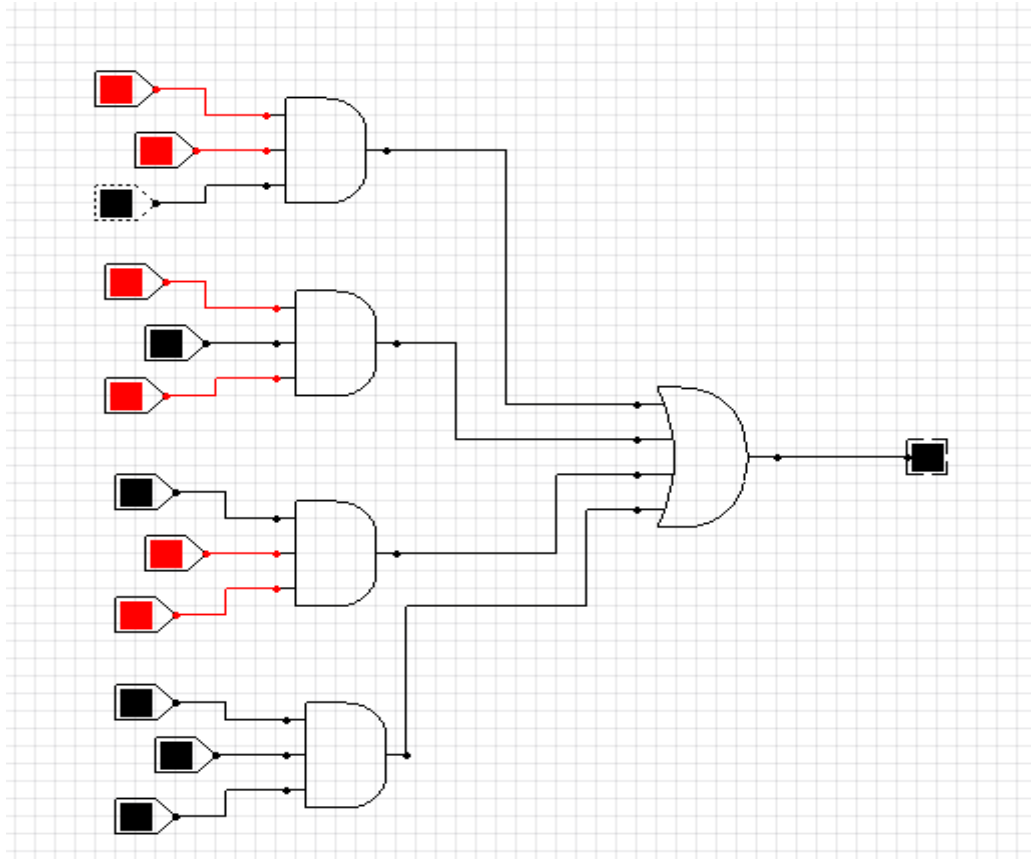

$$S = X'Y'Z + X'YZ' + XY'Z' + XYZ$$

 A full adder can be implemented with two half adders and one OR gate. An example is given below:



Here, the S (sum) output from the second half-adder is the exclusive-OR (XOR) of Z and the output of the first half adder giving;

$$S = XY'Z' + X'YZ' + XYZ + X'Y'Z$$

$$C = XY'Z + X'YZ + XY$$